

# CPSC 121: Models of Computation

## Unit 1: Propositional Logic

George Tsiknis

Based on slides by Patrice Belleville and Steve Wolfman

## Pre-Lecture Learning Goals

- By the start of the class, you should be able to:
  - Translate back and forth between simple natural language statements and propositional logic.
  - Evaluate the truth of propositional logic statements using truth tables.
  - Translate back and forth between propositional logic statements and circuits that assess the truth of those statements.

Unit 1 - Propositional Logic

2

## Quiz 1 Feedback



- We will discuss the open-ended question a bit later.

Unit 1 - Propositional Logic

3

## In-Class Learning Goals

- By the end of this unit, you should be able to:
  - Build computational systems to solve real problems, using both propositional logic expressions and equivalent digital logic circuits.
    - The light switches problem from the 1st online quiz.
    - The 7- or 4-segment LED displays we will discuss in class.
- Building ground work for the Course Big Goals:
  - How do we model computational systems?
  - How do we build devices to compute?

Unit 1 - Propositional Logic

4

## Making a Truth Table


- Note: when you write a truth table, always list the combinations in the same order.
  - For instance, with 3 variables
    - the first column contains 4 false followed by 4 true.
    - the second column contains 2 false, 2 true, 2 false, 2 true.
    - and the third column alternates false with true.
  - With  $k$  variables, the first column has  $2^{k-1}$  false and then  $2^{k-1}$  true, the second column has  $2^{k-2}$  false and then  $2^{k-2}$  true (twice), etc.
- Another way is to
  - start with the last column and one variable which will be assigned F and T
  - add one variable at a time duplicating what you have so far and setting the new variable to F for the first copy and T for the second

## Circuits to Logic Expressions

- How do we find the logical expression that corresponds to a circuit's output?
  - First we write the operator for the gate that produces the circuit's output.
  - The operator's left argument is the expression that corresponds to the circuit for the first input of that gate.
  - The operator's right argument is the expression that corresponds to the circuit for the second input of that gate.
  - Build the logical expression for the left and right argument the same way.

## Example 1


- What does this circuit compute?

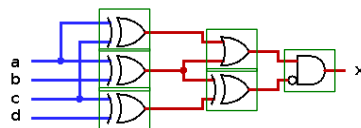

$$((a \oplus c) \vee (a \oplus b)) \wedge \neg((a \oplus b) \oplus c \oplus d)$$

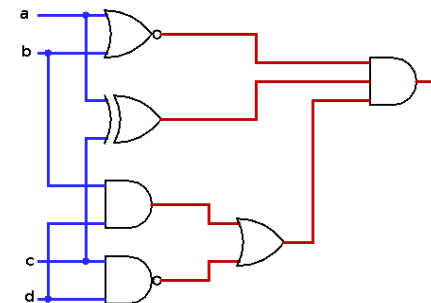
## Example 2

- What logical expression corresponds to the following circuit?



## Problem: Three-Switch

- Design a circuit that changes the state of the light whenever any of the switches that control it is flipped.
- Ideally your solution would work with any number!

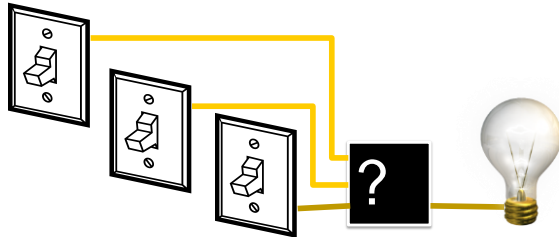

Unit 1 - Propositional Logic

9

## How do we approach this?



- **Try to understand the “story”:**
  - what are the inputs and outputs?
- **Formalize the problem:**
  - “Let a,b,c represent 3 switches from left to right”
- **Solve in propositional logic:**
  - may create a truth table with the inputs and outputs
- **Try a simpler problem:**
  - start with 1 switch; then try 2; then try 3 switches.
  - see if we can generalize to n switches.
- **Test your answer:**
  - try some cases, or check some properties

Unit 1 - Propositional Logic

10

## One Switch



- Identifying inputs/outputs: consider these:
  - **Input<sub>1</sub>**: the switch flipped
  - **Input<sub>2</sub>**: the switch is on
  - **Output<sub>1</sub>**: the light is on
  - **Output<sub>2</sub>**: the light changed states
- Which are most useful for this problem?
  - Input<sub>1</sub>** and **Output<sub>1</sub>**
  - Input<sub>1</sub>** and **Output<sub>2</sub>**
  - Input<sub>2</sub>** and **Output<sub>1</sub>**
  - Input<sub>2</sub>** and **Output<sub>2</sub>**
  - None of these

Unit 1 - Propositional Logic

11

## One Switch



- Let's use: S = switch is on  
out = light is on
- Truth table:
- Which of the following circuits solves the problem?
  - 1.
  - 2.
  - 3.

Unit 1 - Propositional Logic

12

## Two Switches



- Make sure we understand the problem first.
- Is the light on or off when both switches are “on”?
  - A. On in every correct solution.
  - B. Off in every correct solution.
  - C. Depends, but a correct solution should always do the same thing with the same settings for the switches..
  - D. Depends, and a correct solution might do different things at different times with the same settings for the switches.
  - E. Neither on nor off.

## Two Switches




- Circuit design tip: if you are not sure where to start while designing a circuit,
  - First build the truth table.
  - Then turn it into a circuit.
- For the two switches problem:
  - We can decide arbitrarily what the output is when all switches are OFF.
  - This determines the output for all other cases!
  - Let's see how...
- Truth table (suppose light OFF when all switches are OFF):
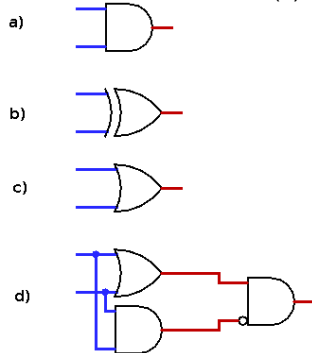
## Two Switches



- Two switches: which circuit(s) work(s) ?



## Three Switches



- Fill in the circuit's truth table:
- Which output column(s) is(are) correct ?

|                |                |                | A   | B   | C   | D   | E            |
|----------------|----------------|----------------|-----|-----|-----|-----|--------------|
| S <sub>1</sub> | S <sub>2</sub> | S <sub>3</sub> | out | out | out | out | None of them |
| T              | T              | T              | T   | F   | F   | T   |              |
| T              | T              | F              | F   | T   | T   | F   |              |
| T              | F              | T              | F   | T   | F   | T   |              |
| T              | F              | F              | T   | F   | T   | F   |              |
| F              | T              | T              | F   | T   | F   | T   |              |
| F              | T              | F              | T   | F   | T   | F   |              |
| F              | F              | T              | T   | F   | F   | T   |              |
| F              | F              | F              | F   | T   | T   | F   |              |

## Three Switches



- Suppose we decided to have the light OFF when all switches are OFF. What pattern do we observe?
  - The light is ON if
- What is the formula for it?
  -
- Now to generalize to  $n$  switches...
  - What do you think the answer is?
  -
- How can we convince ourselves that it is correct?
  - Mathematical induction


Unit 1 - Propositional Logic

17

## 7-Segment LED Display



- **Problem:** design a circuit that displays the numbers 0 through 9 using seven LEDs (lights) in the shape illustrated below.

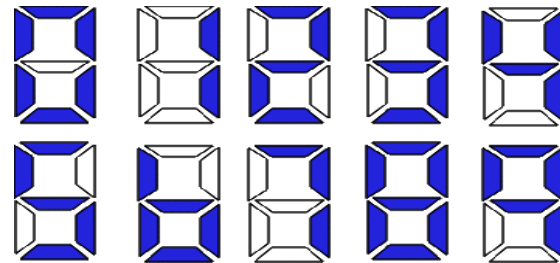

Unit 1 - Propositional Logic

18

## 7-Segment LED Display



- Understanding the story:  
How many inputs *to our circuit* are there?
- a. One
- b. Seven
- c. Ten
- d. Four
- e. None of these

Unit 1 - Propositional Logic

19

## 7-LED Display



- **Problem:** Design a circuit that displays the numbers 0 through 9 using seven LEDs (lights) in the shape illustrated above.
- **First: what's the circuit's job?**
  -

20

## 7-LED Display-Input **Values**



- How many different values (messages) must the circuit understand?  
(This is **different than** “how many inputs are there”.)

- a. One
- b. Seven
- c. Ten
- d. Four
- e. None of these

21

## 7-LED Display-Input **Lines**



- How many different “parameters” (wires) carry those messages?  
(Not *quite* parameter like in CPSC 110... more like an input wire).

- a. One
- b. Seven
- c. Ten
- d. Four
- e. None of these

22

## 7-LED Display-Inputs



- How do we represent the inputs?
  - Use ? logical (true/false) values.
  - Each integer represented by 1 specific combination.
  - Could we do this randomly?
    - Yes!
  - But we won't
    - How many of you know about binary representation?
- How many values we can represent with
  - 1 propositional variable :
  - 2 propositional variables :
  - 3       "               "       :
  - n       "               "       :

Unit 1 - Propositional Logic

23

## 7-LED Display-Representing Inputs



- Here's how we will represent the inputs:

| #   | a | b | c | d |
|-----|---|---|---|---|
| 0   | F | F | F | F |
| 1   | F | F | F | T |
| 2   | F | F | T | F |
| 3   | F | F | T | T |
| 4   | F | T | F | F |
| 5   | F | T | F | T |
| 6   | F | T | T | F |
| 7   | F | T | T | T |
| 8   | T | F | F | F |
| 9   | T | F | F | T |
| ... |   |   |   |   |

Notice the order: F's first.

Unit 1 - Propositional Logic

24

## 7-LED Display-Outputs




### Understanding Outputs:

#### How many outputs are there?

- 1
- 4
- 7
- 10
- None of the above
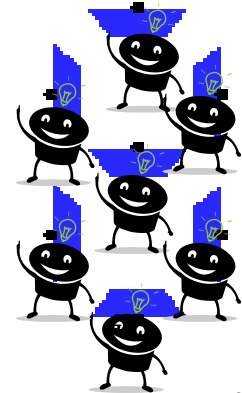
## Simulate 7-LED Display


- Let's simulate it with people (raising their hands) ...
- Which other person's algorithm do you need to know about?
  - No one else's
  - Your neighbours
  - The person opposite to you
  - Everybody else's
  - None of the above.



## Analyzing One Segment

### What's the truth table for the lower-left segment?

| # | a | b | c | d | a. | b. | c. | d. | e.             |
|---|---|---|---|---|----|----|----|----|----------------|
| 0 | F | F | F | F | F  | F  | F  | F  | None of these. |
| 1 | F | F | F | T | T  | T  | F  | F  |                |
| 2 | F | F | T | F | F  | F  | T  | 6  |                |
| 3 | F | F | T | T | T  | T  | F  | 8  |                |
| 4 | F | T | F | F | F  | T  | F  | 4  |                |
| 5 | F | T | F | T | T  | T  | F  | 7  |                |
| 6 | F | T | T | F | F  | F  | T  | 9  |                |
| 7 | F | T | T | T | T  | T  | F  | 3  |                |
| 8 | T | F | F | F | F  | F  | T  | 1  |                |
| 9 | T | F | F | T | T  | T  | F  | 5  |                |

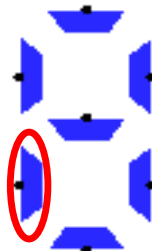

## Analyzing One Segment



- From the truth table, we can make an expression for each true row and OR them together.

| # | a | b | c | d | out |
|---|---|---|---|---|-----|
| 0 | F | F | F | F | T   |
| 1 | F | F | F | T | F   |
| 2 | F | F | T | F | T   |
| 3 | F | F | T | T | F   |
| 4 | F | T | F | F | F   |
| 5 | F | T | F | T | F   |
| 6 | F | T | T | F | T   |
| 7 | F | T | T | T | F   |
| 8 | T | F | F | F | T   |
| 9 | T | F | F | T | F   |

Which logical statement is true only in this row?

- $\sim a \vee \sim b \vee c \vee \sim d$
- $a \wedge b \vee c \wedge d$
- $\sim a \wedge \sim b \wedge c \wedge \sim d$
- $a \wedge b \wedge \sim c \wedge d$
- None of these

## Analyzing One Segment

- Let's complete the expression for the lower-left segment

| # | a | b | c | d | out |         |
|---|---|---|---|---|-----|---------|
| 0 | F | F | F | F | T   | ← ( ) ✓ |
| 1 | F | F | F | T | F   |         |
| 2 | F | F | T | F | T   | ← ( ) ✓ |
| 3 | F | F | T | T | F   |         |
| 4 | F | T | F | F | F   |         |
| 5 | F | T | F | T | F   | ← ( ) ✓ |
| 6 | F | T | T | F | T   | ← ( )   |
| 7 | F | T | T | T | F   |         |
| 8 | T | F | F | F | T   | ← ( )   |
| 9 | T | F | F | T | F   |         |

29

## Alternative to Table with Many Ts

- We can use the F rows and negate the statement!

| # | a | b | c | d | out |
|---|---|---|---|---|-----|
| 0 | F | F | F | F | T   |
| 1 | F | F | F | T | T   |
| 2 | F | F | T | F | T   |
| 3 | F | F | T | T | T   |
| 4 | F | T | F | F | T   |
| 5 | F | T | F | T | F   |
| 6 | F | T | T | F | F   |
| 7 | F | T | T | T | T   |
| 8 | T | F | F | F | T   |
| 9 | T | F | F | T | T   |

Which of these correctly models this LED?

- $\sim(\sim a \wedge b \wedge \sim c \wedge d) \vee \sim(\sim a \wedge b \wedge c \wedge \sim d)$
- $\sim(a \wedge \sim b \wedge c \wedge \sim d) \vee \sim(a \wedge \sim b \wedge \sim c \wedge d)$
- $\sim[(\sim a \wedge b \wedge \sim c \wedge d) \vee (\sim a \wedge b \wedge c \wedge \sim d)]$
- $\sim[(a \wedge \sim b \wedge c \wedge \sim d) \vee (a \wedge \sim b \wedge \sim c \wedge d)]$
- None of these

30

## Another Way

| # | a | b | c | d | out |
|---|---|---|---|---|-----|
| 0 | F | F | F | F | T   |
| 1 | F | F | F | T | F   |
| 2 | F | F | T | F | T   |
| 3 | F | F | T | T | F   |
| 4 | F | T | F | F | F   |
| 5 | F | T | F | T | F   |
| 6 | F | T | T | F | T   |
| 7 | F | T | T | T | F   |
| 8 | T | F | F | F | T   |
| 9 | T | F | F | T | F   |

- Looking back at the bottom-left segment:

- There may be a simpler proposition, which will translate into a smaller circuit.
- Can you find a pattern in the rows for which the segment should be "on"?

Unit 1 - Propositional Logic

31

## What is coming up?

- Second online quiz: due **SUNDAY, Jan 12, 7:00pm.**
- Assigned reading for the quiz:
  - Epp, 4th edition: 2.2
  - Epp, 3rd edition: 1.2
  - Rosen, 6th edition: 1.1 from page 6 onwards.

Unit 1 - Propositional Logic

32



## Exercises:

- Prove that our two solutions for the lower-left segment are not logically equivalent.
  - You should do this by providing values for the variables, so the two propositions have different truth values.
  - Why are they both correct solutions, despite that?
- Finish the problem by building circuits for the other 5 segments.
- Design a circuit that takes three bits as input, and outputs the binary representation for their sum.